

CS2100 Comp Org Notes

AY23/24 Sem 1, github.com/gerreck

12. Boolean Algebra

Digital Circuits

- Two voltage levels, 1 for high, 0 for low.
- Digital circuits over analog circuits are more reliable, specified accuracy (determinable).
- Digital circuits abstracted using simple mathematical model: **(Boolean Algebra)**
- Design, Analysis and simplification of digital circuit: **Digital Logic Design.**
- Combinational:** no memory, output depends solely on the input. (gates, adders, multiplexers)
- Sequential:** with memory, output depends on both input and current state. (counters, registers, memories)

Boolean Algebra

connectives in order of precedence:

- negation** A' equivalent to **NOT**
- conjunction** $A \cdot B$ equivalent to **AND**
- disjunction** $A + B$ equivalent to **OR**
- Note: always write the AND operator \cdot , do not omit, as it may be confused with a 2 bit value, AB .
- Truth Table:** Provides listing of every possible combination of inputs and corresponding outputs. We may prove using truth table by comparing columns.

Duality

- Duality:** if the AND/OR operators and identity elements 0/1 interchanged in a boolean equation, it remains valid.
- e.g. the dual equation of $a + (b \cdot c) = (a + b) \cdot (a + c)$ is $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$, where if one is valid, then its dual is also valid.

Laws & Theorems of Boolean Algebra

Identity laws	
$A + 0 = 0 + A = A$	$A \cdot 1 = 1 \cdot A = A$
Inverse/complement laws	
$A + A' = A' + A = 1$	$A \cdot A' = A' \cdot A = 0$
Commutative laws	
$A + B = B + A$	$A \cdot B = B \cdot A$
Associative laws *	
$A + (B + C) = (A + B) + C$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$
Distributive laws	
$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$

Idempotency	
$X + X = X$	$X \cdot X = X$
One element / Zero element	
$X + 1 = 1 + X = 1$	$X \cdot 0 = 0 \cdot X = 0$
Involution	
$(X')' = X$	
Absorption 1	
$X + X \cdot Y = X$	$X \cdot (X + Y) = X$
Absorption 2	
$X + X' \cdot Y = X + Y$	$X \cdot (X' + Y) = X \cdot Y$
DeMorgans' (can be generalised to more than 2 variables)	
$(X + Y)' = X' \cdot Y'$	$(X \cdot Y)' = X' + Y'$
Consensus	
$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$

left/right equations are duals of each other

Proving Theorems

- Theorems can be proved using truth table, or by algebraic manipulation using other theorems/laws.

* Example: Prove absorption theorem $X + X \cdot Y = X$

$X + X \cdot Y$
= $X \cdot 1 + X \cdot Y$ (by identity law)
= $X \cdot (1 + Y)$ (by distributivity)
= $X \cdot 1$ (by one element law)
= X (by identity law)

* By the principle of duality, we may also cite (without proof) that $X \cdot (X + Y) = X$.

Boolean Functions, Complements

- Represented by F , e.g. $F1(x, y, z) = x \cdot y \cdot z'$.
- To prove $F1 = F2$, we may use boolean algebra, or use truth tables.
- Complement Function is denoted as F' , obtained by interchanging 1 with 0 in function's output values.

Standard Forms

- Literals:** A Boolean variable on its own or in its complemented form. (e.g. x, x')
- Product Term:** A single literal or a logical product (AND, \cdot) of several literals. (e.g. $x, x \cdot y \cdot z'$)
- Sum Term:** A single literal or a logical sum (OR $+$) of several literals. (e.g. $A + B'$)
- sum-of-products (SOP) expression:** A product term or a logical sum (OR $+$) of several product terms.
- product-of-sums (POS) expression:** A sum term or a logical product (AND) of several sum terms.
- Every boolean expr can be expressed in SOP/POS form.

Minterms and Maxterms

- minterm** (of n variables): a product term that contains n literals from all the variables; denoted m_0 to $m[2^n - 1]$
- maxterm** (of n variables): a sum term that contains n literals from all the variables; denoted M_0 to $M[2^n - 1]$
- Each minterm is the complement ($m_{2'} = M_2$) of its corresponding maxterm, vice versa.

x	y	Minterms		Maxterms	
		Term	Notation	Term	Notation
0	0	$x' \cdot y'$	m_0	$x + y$	M_0
0	1	$x' \cdot y$	m_1	$x + y'$	M_1
1	0	$x \cdot y'$	m_2	$x' + y$	M_2
1	1	$x \cdot y$	m_3	$x' + y'$	M_3

Canonical Forms

- Canonical/normal form: a unique form of representation.
- Sum-of-minterms** = Canonical sum-of-products
- Product-of-maxterms** = Canonical product-of-sums

Given truth tables

x	y	z	F1	F2	F3
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	1	1
1	1	0	1	1	0
1	1	1	0	1	0

Sum of minterms $0 \rightarrow x'$
 $1 \rightarrow x$

$F1 = x \cdot y \cdot z' = m_6$
 $F2 = x' \cdot y' \cdot z + x' \cdot y \cdot z' + \dots$
 $= m_0 + m_4 + m_5 + m_7$
 $= \sum m(0, 4, 5, 7)$
 $F3 = m_1 + m_2 + m_4 + m_5$
 $= \sum(1, 2, 4, 5) \rightarrow \sum(1, 2-5)$

Product of Maxterms

$F2 = \prod m(0, 2, 3)$
 $F3 = \prod m(0, 2, 6, 7)$

- We can convert between sum-of-minterms and product-of-maxterms easily, by DeMorgan's.

13. Logic Gates & Simplification

Logic Gates

- Fan-in: The number of inputs of a gate $\geq 1, 2$.
- Implement bool exp / function as logic circuit.

Universal Gates

- **universal gate**: can implement a complete set of logic.
- $\{AND, OR, NOT\}$ are a complete set of logic, sufficient for building any boolean function.
- $\{NAND\}$ and $\{NOR\}$ themselves a complete set of logic. Implement NOT/AND/OR using only NAND or NOR gates.

SOP and POS

- an SOP expression can be easily implemented using
 - 2-level AND-OR circuit or 2-level NAND circuit
- a POS expression can be easily implemented using
 - 2-level OR-AND circuit or 2-level NOR circuit

Algebraic Simplification

- **Function Simplification**: Make use of algebraic (using theorems) or Karnaugh Maps (easier to use, limited to no more than 6 variables) or Quine-McCluskey.
- **Algebraic Simplification**: aims to minimise
 1. number of literals (prioritised over number of terms)
 2. number of terms.


Half Adder

- Half adder is a circuit that adds 2 single bits (X, Y) to produce a result of 2 bits (C, S).

$$\begin{aligned} C &= X \cdot Y; \\ S &= X \oplus Y \end{aligned}$$

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

outputs

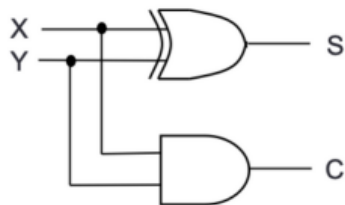


implementation of a half adder

Universal Gates


Gate Symbols




AND Gate

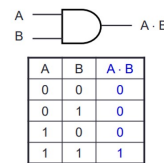


OR Gate

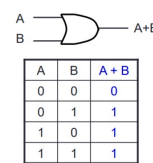


(NOT gate)

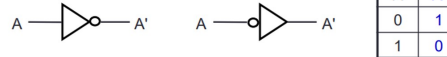


NAND gate

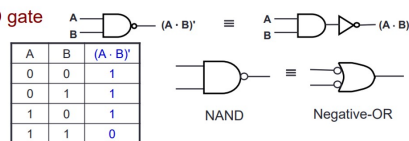


NOR gate

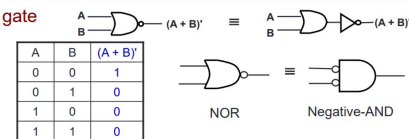

XOR gate

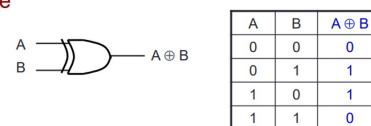


XNOR gate

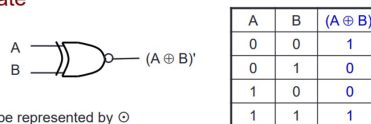

XNOR can be represented by \odot (Example: $A \odot B$)

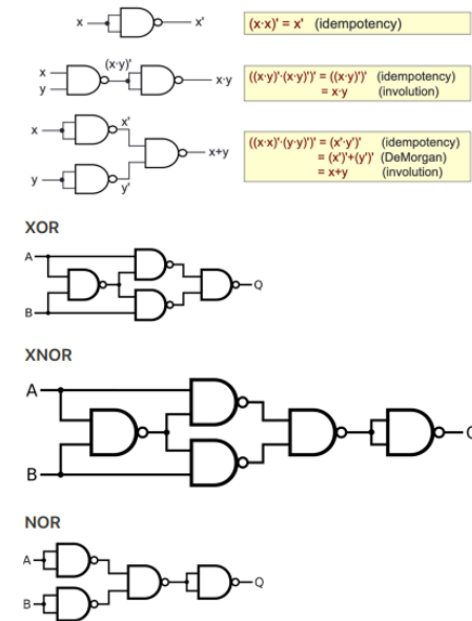
NAND as Universal Gate (Complete Logic Set)



NOR as Universal Gate (Complete Logic Set)

NOR

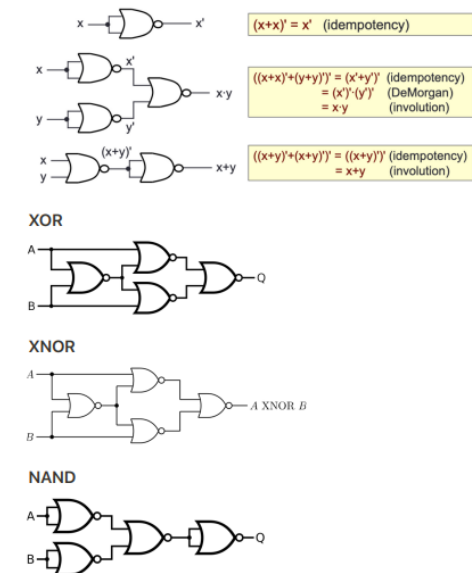• Proof: Implement NOT/AND/OR using only NOR gates.



Gray Code


- Only a **single bit change** from one code value to the next. 4 bit standard gray code:

Decimal	Binary	Gray Code	Decimal	Binary	Gray code
0	0000	0000	8	1000	1100
1	0001	0001	9	1001	1101
2	0010	0011	10	1010	1111
3	0011	0010	11	1011	1110
4	0100	0110	12	1100	1010
5	0101	0111	13	1101	1011
6	0110	0101	14	1110	1001
7	0111	0100	15	1111	1000

- not restricted to decimal digits: n bits can have up to 2^n values.
- aka reflected binary code. To generate gray code, reflect.
- not unique - multiple possible Gray code sequences

K Maps

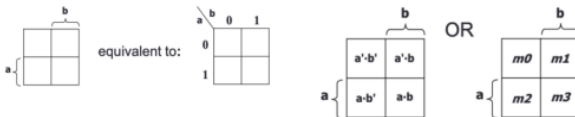- Simplify (SOP) expressions, with fewest possible product terms and literals.
- Based on **Unifying Theorem** ($A + A' = 1$), **complement law**.
- Abstract form of Venn diagram, matrix of squares, each square represents a **minterm**.
- Two adjacent squares represent minterms that differ by exactly one literal.



K Map for a function:

- The K-map for a function is filled by putting:
 - A '1' in the square the corresponds to a **minterm**
 - A '0' otherwise
- Each **valid grouping** of adjacent cells containing '1' corresponds to a simpler product term.
- Group must have width/length (size) in **powers of 2**.
- larger group** = fewer literals in result product term
- fewer groups** = fewer product terms in final SOP exp.
- Group maximum cells, and select fewest groups.

K-Maps

3-Variable

bc	00	01	11	10
a				
0	m0	m1	m3	m2
1	m4	m5	m7	m6


4-Variable

yz	00	01	11	10
wx				
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

5-Variable

yz	00	01	11	10
wx				
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

Valid Groupings

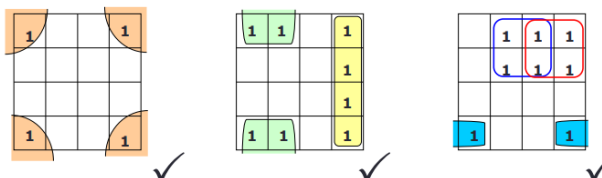

6-Variable

ef	00	01	11	10
cd				
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

Using a K-map

- K-map of function easily filled in when function in sum-of-minterms form.
- If not in sum-of-minterms, convert into sum-of-products (SOP) form, expand SOP expr into sum-of-minterms, or fill directly based on SOP.

(E)PIs

- implicant**: product term that could be used to cover minterms of the function.
- prime implicant**: a product term obtained by combining the maximum possible number of minterms from adjacent squares in the map.
- essential prime implicant**: a prime implicant that includes at least one minterm that is not covered by any other prime implicant

K-maps to find POS

- shortcut: group maxterms (0s) of given function
- long way: 1. convert K-map of F to K-map of F' (by flipping 0/1s), 2. get SOP of F' $POS=(SOP)'$.

Don't-Care Conditions

- denoted d , e.g.:
- $$F(A, B, C) = \sum m(3, 5, 6) + \sum d(0, 7)$$